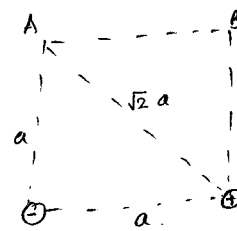


Prob. 1

$$(a) \quad V_A = -\frac{kq}{a} + \frac{kq}{\sqrt{2}a} = -\frac{kq}{a} \left(1 - \frac{1}{\sqrt{2}}\right)$$

$$= -\frac{8.99 \times 10^9 \times 5.00 \times 10^{-9} \text{ C}}{5.00 \times 10^{-2} \text{ m}} \left(1 - \frac{1}{\sqrt{2}}\right) = -263 \text{ V}$$



$$(b) \quad V_B = -\frac{kq}{\sqrt{2}a} + \frac{kq}{a} = +\frac{kq}{a} \left(1 - \frac{1}{\sqrt{2}}\right) = +263 \text{ V}$$

$$(c) \quad V_B - V_A = +263 - (-263) = +527 \text{ V}$$

$$(d) \quad \Delta U = Q \Delta V$$

$$= Q (V_B - V_A) = 2.00 \times 10^{-6} \text{ C} \times 527 \text{ V}$$

$$= 1.05 \text{ mJ}$$

Prob. 2

$$V = a + bx^2$$

$$\vec{E} = -\hat{i} \frac{\partial V}{\partial x} - \hat{j} \frac{\partial V}{\partial y} - \hat{k} \frac{\partial V}{\partial z}$$

$$= -\hat{i} 2bx - \hat{j} 0 - \hat{k} 0$$

$$= -\hat{i} 2 \left(-450 \frac{\text{V}}{\text{cm}^2}\right) 2.00 \text{ cm}$$

$$= -\hat{i} 1800 \frac{\text{V}}{\text{cm}}$$

Magnitude :  $1800 \frac{\text{V}}{\text{cm}}$

Direction : along negative  $\hat{x}$ .

$$\frac{\partial V}{\partial x} = 2bx$$

$$\frac{\partial V}{\partial y} = 0$$


$$\frac{\partial V}{\partial z} = 0$$

Prob. 3

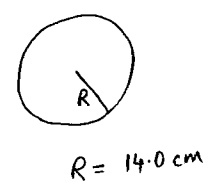(a)  $r = 8.0 \text{ cm} < R = 14.0 \text{ cm}$

Potential inside a conductor is equal to the potential on the surface of a conductor.

$$V = \frac{kQ}{R} = \frac{8.99 \times 10^9 \times 8.0 \times 10^{-6}}{14.0 \times 10^{-2}} = 5.14 \times 10^5 \text{ V}$$



(b)  $r = 16.0 \text{ cm} > R = 14.0 \text{ cm}$

$$V = \frac{kQ}{r} = \frac{8.99 \times 10^9 \times 8.0 \times 10^{-6}}{16.0 \times 10^{-2}} = 4.50 \times 10^5 \text{ V}$$

Prob. 4

$$\begin{aligned} \text{Cost} &= \left( 0.12 \frac{\text{USD}}{\text{kWh}} \right) \times (\text{Energy consumed in 2 weeks}) \\ &= \left( 0.12 \frac{\text{USD}}{10^3 \text{ kWh}} \right) \times (100.0 \text{ W} \times 14 \times 24 \text{ h}) \\ &= 0.12 \times \frac{1}{10^3} \times 100.0 \times 14 \times 24 \text{ USD} \\ &= 4.03 \text{ USD} \end{aligned}$$

$$\text{Power} = \frac{\text{Energy}}{\text{Time}}$$

Prob. 5

$$\begin{aligned} \frac{1}{R_{eq}} &= \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \\ &= \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R} \end{aligned}$$


$$R_1 = R_2 = \dots = R_n = R = 200.0 \Omega$$

$$\begin{aligned} \frac{1}{R_{eq}} &= \frac{100}{R} \\ \Rightarrow R_{eq} &= \frac{R}{100} = \frac{200.0 \Omega}{100} = 2.00 \Omega \end{aligned}$$

Prob. 6.

$$(a) \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{1.00} + \frac{1}{2.00} = \frac{3}{2.00}$$

$$\Rightarrow C_{eq} = 0.667 \mu F$$

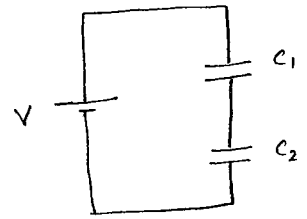

$$(b) Q_1 = Q_2 = Q = V C_{eq} = 10.0 \times 0.667 \mu = 6.67 \mu C$$

$$(c) V_1 = \frac{Q_1}{C_1} = \frac{6.67 \mu C}{1.00 \mu F} = 6.67 V$$

$$V_2 = \frac{Q_2}{C_2} = \frac{6.67 \mu C}{2.00 \mu F} = 3.33 V$$

Prob. 7

loop abcfa:

$$+ V_1 - I_1 R_1 - I_3 R_3 = 0$$

$$+ 10 - I_1 100 - (I_1 + I_2) 300 = 0$$

$$40 I_1 + 30 I_2 = 1$$

loop edcfe:


$$+ V_2 - I_2 R_2 - I_3 R_3 = 0$$

$$+ 20 - I_2 200 - (I_1 + I_2) 300 = 0$$

$$30 I_1 + 50 I_2 = 2$$

$$I_3 = I_1 + I_2 = -9.09 + 45.5 = +36.4 \text{ mA}$$

Direction: from c → f.

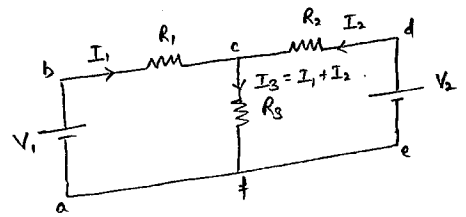

$$40 I_1 + 30 I_2 = 1$$

$$30 I_1 + 50 I_2 = 2$$

$$I_1 = \frac{1 \times 50 - 2 \times 30}{40 \times 50 - 30 \times 30} = -9.09 \text{ mA}$$

$$I_2 = \frac{40 \times 2 - 30 \times 1}{40 \times 50 - 30 \times 30} = +45.5 \text{ mA}$$

Prob. 8

(a)  $+V - IR - \frac{Q}{C} = 0$

(b) Maximum charge =  $Q(\infty) = CV$

$Q(t) = CV [1 - e^{-\frac{t}{RC}}]$

$0.70 CV = CV [1 - e^{-\frac{t}{RC}}]$

$0.70 = 1 - e^{-\frac{t}{RC}}$

$e^{-\frac{t}{RC}} = 1 - 0.70 = 0.30$

$\ln e^{-\frac{t}{RC}} = \ln 0.30$

$-\frac{t}{RC} = \ln 0.30$

$t = -RC \ln 0.30$

$= -30.0 \times 10^3 \Omega \times 10.0 \times 10^{-6} F \ln(0.30)$

$= 0.361 \text{ seconds.}$