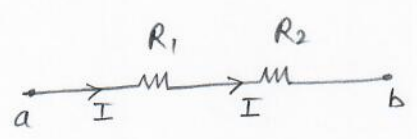


# Solutions

## Problem 1

$$V_a - V_b = I(R_1 + R_2)$$

$$I = \frac{(4.5) - (-1.5)}{(1.0 + 2.0) \times 10^3} = 2.0 \text{ mA}$$



2.0 mA in each resistor, from a to b.

## Problem 2

Left circuit:  $R_{eq} = 2R$

Right circuit:  $R_{eq} = R + \left[ \frac{1}{\frac{1}{2R} + \left\{ R + \frac{1}{\left( \frac{1}{2R} + \frac{1}{R+R} \right)} \right\}} \right]$


$$= R + \left[ \frac{1}{\frac{1}{2R} + \{R + R\}} \right]$$

$$= R + 2R$$

$$= 2R$$

Both circuits have the same equivalent resistance of  $2R$ .

## Problem 3

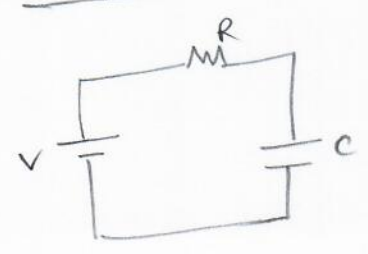

An application is in the design of camera flash.

Problem 4

Circle.

Problem 5

$$V_a = \frac{kq}{\left(\frac{\sqrt{2}L}{2}\right)} + \frac{kq}{\left(\frac{\sqrt{2}L}{2}\right)} + \frac{kq}{\left(\frac{\sqrt{2}L}{2}\right)} + \frac{kq}{\left(\frac{\sqrt{2}L}{2}\right)} = 4 \frac{kq}{L} \frac{2}{\sqrt{2}} = 4\sqrt{2} \frac{kq}{L}$$

$$V_b = \frac{kq}{\left(\frac{L}{2}\right)} + \frac{kq}{\left(\frac{L}{2}\right)} + \frac{kq}{\left(\frac{\sqrt{5}L}{2}\right)} + \frac{kq}{\left(\frac{\sqrt{5}L}{2}\right)} = \frac{kq}{L} \left[ 2 + 2 + \frac{2}{\sqrt{5}} + \frac{2}{\sqrt{5}} \right]$$
$$= \frac{kq}{L} 4 \left( 1 + \frac{1}{\sqrt{5}} \right)$$

$$V_a - V_b = \frac{kq}{L} \left[ 4\sqrt{2} - 4 \left( 1 + \frac{1}{\sqrt{5}} \right) \right] \approx -0.132 \frac{kq}{L}$$


Problem 6

$$\frac{1}{C_4} = \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{20.0} + \frac{1}{30.0} = \frac{50.0}{600.}$$

$$C_4 = 12.0 \text{ nF}$$

$$Q_4 = C_4 V = (12.0 \text{ nF})(10.0 \text{ V})$$
$$= 120. \text{ nC}$$

$$Q_2 = Q_4 = 0.120 \mu\text{C}$$

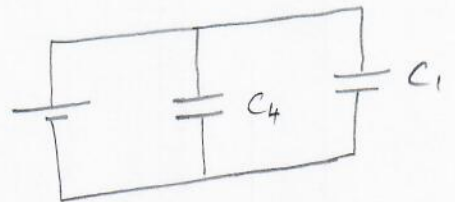

Problem 7

$$R' = \frac{\rho l'}{A'} \quad l' = 2l$$
$$= \frac{\rho(2l)}{\left(\frac{A}{2}\right)} = 4 \frac{\rho l}{A} = 4R.$$

$$l'A' = Al$$
$$2l \left(\frac{A}{2}\right) = Al$$
$$A' = \frac{A}{2}$$


Problem 8

loop fcdfe:

$$+V_2 - I_2 R_2 = 0$$

$$+20.0 = I_2(200.)$$
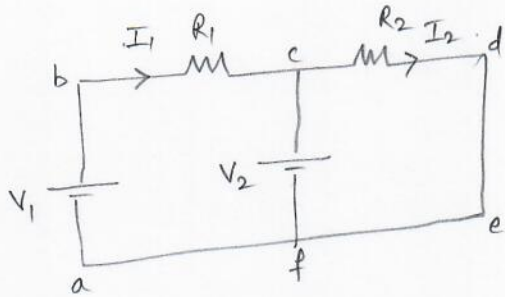
$$I_2 = 0.100 \text{ A}$$
$$= 1.00 \text{ mA}$$



loop abcfa:

$$+V_1 - I_1 R_1 - V_2 = 0$$

$$+10.0 - I_1(100.) - 20.0 = 0$$

$$I_1 = -0.100 \text{ A} = -1.00 \text{ mA}$$

$I_2$  is 1.00 mA from c  $\rightarrow$  d.  
 $I_1$  is 1.00 mA from c  $\rightarrow$  b.