

Solution

PHYS-205B-002

(Midterm Exam 02)


Spring 2025

①

Problem 1

Electric potential decreases as we go closer to a negative charge.

$$V = - \frac{k|Q|}{r}$$

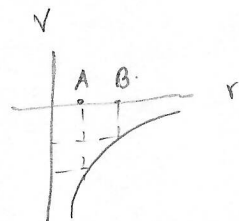

⇒ Point B is at higher potential relative to point A.

Problem 2

Points a, b, and c, have the same potential, relative to d. Thus, resistors R_1 , R_2 , and R_3 , are in parallel.

$$\frac{1}{R_{eq}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R}$$

$$\Rightarrow R_{eq} = \frac{R}{3}$$

Problem 3

$$\text{Energy} = (\text{Power})(\text{time})$$

$$= \left(12 \frac{\text{J}}{\text{s}}\right) (365 \times 24 \times 60 \times 60 \text{ s}) = 3.8 \times 10^8 \text{ J}$$

Problem 4

$$[RC] = \frac{[V]}{[I]} \frac{[Q]}{[V]} = [t] = T$$

dimension of time.

$$V = IR$$

$$V = \frac{Q}{C}$$

$$I = \frac{Q}{t}$$

Problem 5


$$V_e = \frac{kq_1}{s} + \frac{kq_2}{s} + \frac{kq_3}{s} + \frac{kq_4}{s}$$

$$= \frac{k}{s} (q_1 + q_2 + q_3 + q_4)$$

$$= \frac{kq}{s} (+1 - 2 - 3 + 3)$$

$$= - \frac{kq}{s} = - \frac{kq}{(L/2)}$$

$$= -4.2 \text{ Volt}$$

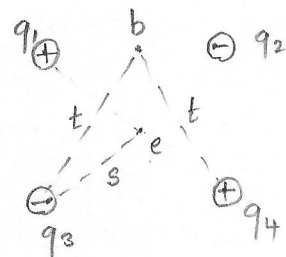

$$s = \sqrt{\left(\frac{L}{2}\right)^2 + \left(\frac{L}{2}\right)^2} = \frac{L}{2}\sqrt{2}$$

$$V_b = \frac{kq_1}{L/2} + \frac{kq_2}{L/2} + \frac{kq_3}{t} + \frac{kq_4}{t}$$

$$= kq \left[+\frac{1}{L/2} - \frac{2}{L/2} + \frac{3}{t} - \frac{3}{t} \right]$$

$$= - \frac{kq}{(L/2)} = - \frac{(9.0 \times 10^9)(1.0 \times 10^{-9})}{(6.0/2)} = -3.0 \text{ Volt.}$$

$$V_b - V_e = -3.0 - (-4.2) = 1.2 \text{ Volt.}$$


Problem 6

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{1.0} + \frac{1}{2.0} \Rightarrow C = \frac{2.0}{3.0} \mu F = 0.67 \mu F$$

$$Q = Q_1 = Q_2 = VC = 6.7 \mu C$$

$$U_1 = \frac{Q_1^2}{2C_1} = \frac{(6.7 \times 10^{-6})^2}{2(1.0 \times 10^{-6})} = 23 \mu J$$

$$U_2 = \frac{Q_2^2}{2C_2} = 12 \mu J$$

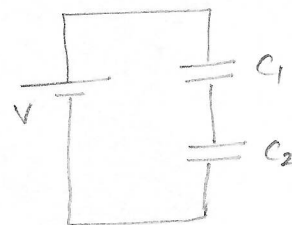

Problem 7

junction c: $I_1 = I_2 + I_3$ — (i)

loop abcfa:

$$+V_1 - I_1 R_1 - I_3 R_3 = 0$$

$$+10. - 10. (I_2 + I_3) - 30. I_3 = 0$$

$$10. I_2 + 40. I_3 = 10. \quad \text{— (ii)}$$

loop fcd ef:

$$+ I_3 R_3 - I_2 R_2 = 0$$

$$30. I_3 = 20. I_2$$

$$I_2 = 1.5 I_3 \quad \text{— (iii)}$$

Using (iii) in (ii)

$$10. (1.5 I_3) + 40. I_3 = 10.$$

$$55 I_3 = 10.$$

$$\Rightarrow I_3 = 0.18 \text{ A} \quad \text{— (iv)}$$

Using (iv) in (iii)

$$I_2 = 1.5 (0.18) = 0.27 \text{ A} \quad \text{— (v)}$$

Using (iv) and (v) in (i)

$$I_1 = 0.27 + 0.18 = 0.45 \text{ A}.$$

